

# Modified T-coil Network

JIM HAGERMAN, Hughes-JVC Technology Corp., 2310 Camino Vida Roble, Carlsbad, CA 92009;  
Internet: 72230.1704@compuserve.com

9/12/95

The interface between two amplifiers or circuits can often lead to bandwidth limiting. Figure 1 shows a typical situation where the output current of an amplifier is converted to a voltage by a load resistance and the input capacitance of the following stage. The -3dB bandwidth is given by

$$f_{3dB} = \frac{1}{2pR_L C_L}$$

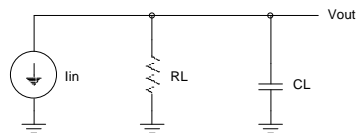


Figure 1. Typical RC network.

Many years ago Tektronix developed an interface network called a bridged T-coil which has some outstanding properties. When the component values are chosen appropriately, the input impedance is perfectly resistive ( $R_L$ ) at all frequencies — no more capacitive loading on the driving amplifier. In addition, output bandwidth is increased by a factor of 2.5 over the circuit of Figure 1. The difficulty with T-coil design is the construction of the transformer formed by  $L_1$  and  $L_2$ . The fractional magnetic coupling must be set precisely for proper operation. Design equations from Tektronix are given as

$$L_1 = \frac{C_L}{4} \left[ 1 + \frac{1}{4Z^2} \right] (R_L + R_S)^2 - R_L R_S C_L - L_S$$

$$L_2 = \frac{C_L}{4} \left[ 1 + \frac{1}{4Z^2} \right] (R_L + R_S)^2 - L_S$$

$$M = \frac{C_L}{4} \left[ R_L^2 - R_S^2 - \frac{1}{4Z^2} (R_L + R_S)^2 \right] + L_S$$

$$C_B = \frac{C_L}{16Z^2} \left[ \frac{R_L + R_S}{R_L} \right]^2$$

$$k = \frac{M}{\sqrt{L_1 L_2}}$$

It is desirable to have no magnetic coupling. Then simple low cost fixed value inductors can be used in place of the transformer. The author's modified T-coil adds a series resistance  $R_{comp}$  which is determined by setting  $M$  to zero.  $R_S$  and  $L_S$  model the interconnection parasitics. The new circuit is given in Figure 2.

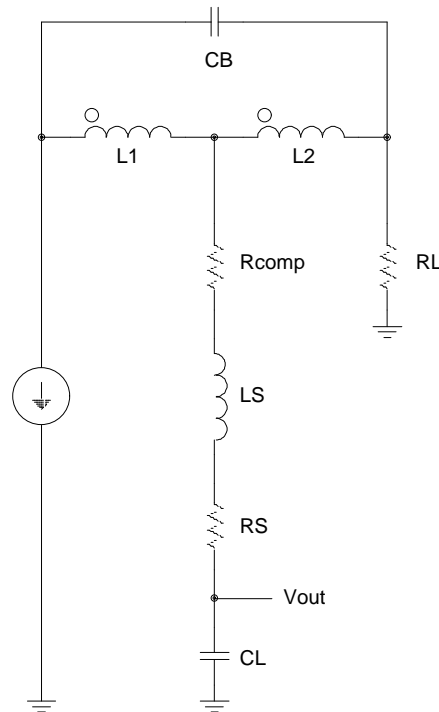


Figure 2. Modified T-coil network.

The solution for  $R_{comp}$  is

$$R_{comp} = \left[ \frac{\sqrt{R_L^2 - (1+4Z^2) \left[ R_L^2 (1-4Z^2) - \left( \frac{16Z^2 L_S}{C_L} \right) \right] - R_L}}{(1+4Z^2)} \right] - R_S$$

The equations for  $L_1$ ,  $L_2$ , and  $C_B$  are the same as before but with  $R_S$  replaced by the quantity  $(R_S + R_{comp})$ . Unfortunately, under some conditions  $R_{comp}$  may calculate as negative or imaginary in which case the modification is not realizable□